CPU Architecture

LAB3 assignment

Digital System Design with VHDL

Hanan Ribo

12/04/2021

Table of contents

1.	Aim of the Task:	3
2.	Assignment definition:	3
	Controller based system:	
	File based simulation of DUT:	
	Requirements:	
	Grading Policy	

1. Aim of the Task:

- System design using concurrent and sequential logic principles using advanced
 Simulation methods (based on material given in LAB1 and LAB2 tasks).
- Controller design based on methodology of Control and Datapath separation.
- Preparation for LAB4 task FPGA based design synthesis of the given design.
- Proper analysis and understanding of architecture design.

2. Assignment definition:

In this task, you are required to design a controller-based system that operates on serial stream of data (operation on series of numbers). The System reads and operates on n numbers in a row:

Input:

$$0, ..., 0, opc, n, x_1, ..., x_n, opc, m, y_1, ..., y_m, opc, k, z_1, ..., z_k, 0, ..., 0$$

Where $opc > 0$; $n > 0$; x_i, y_i, z_i are in 2's complement (can be zero).

Note: the given example contains 3 data sets, without limiting generality.

Output:

$$\prod_{i=1}^{n} x_i, \prod_{i=1}^{m} y_i, \prod_{i=1}^{k} z_i \quad \text{where } \coprod \text{is an ALU operation (except opcode zero)}.$$

Example (given in Decimal for convenience):

Data input:

Data output:

$$0, \dots, 0, 1, 3, 10, 20, 25, 2, 4, 20, 30, 55, 25, 0, \dots, 0$$

$$55, -20$$

3. Controller based system:

 


Figure 1: Overall DUT structure

 


Figure 2: Datapath structure

Decimal	ALUFN	Operation
value		
0	000	ALUout=A
1	001	ALUout=A+B
2	010	ALUout=A-B
3	011	ALUout=A OR B
4	100	ALUout=A AND B
5	101	ALUout=A XOR B

Table 1: ALU Opcodes


 


Figure 3: Control unit structure

 
• The given files that you must use in your project:



- ✓ You can only add code to these files, you are not allowed to erase anything.
- ✓ You can add additional VHDL source code files.
- ✓ Other entities can be designed and modeled behaviorally, structurally, etc.

 4. File based simulation of DUT:

- As depicted in figure 1, in order to simulate the DUT systemly we use file based simulation.
- Input and Output files structure (according the above given example at clause 2):



5. Requirements:

- 1. The design must be well commented.
- 2. Elaborated analysis and wave forms:
 - Remove irrelevant signals.
 - Zoom on regions of interest.
 - Draw clouds on the waveform with explanations of what is happening (Figure 4).
 - Change the waveform colors in ModelSim for clear documentation
 - (Tools->Edit Preferences->Wave Windows).
- 3. A ZIP file in the form of **id1_id2.zip** (where id1 and id2 are the identification number of the submitters, and id1 < id2) *must be upload to Moodle only by student with id1* (any of these rules violation disqualifies the task submission).

4. The **ZIP** file will contain (only the exact next sub folders):

Directory	Contains	Comments
DUT	Project VHDL files	Only VHDL files of DUT, excluding test bench
		Note: your project files must be well compiled
		without errors as a basic condition before
		submission
TB	VHDL files that are used for test bench	One tb.vhd for the Datapath
		One tb.vhd for the Control unit
		One tb.vhd for the overall DUT
SIM	ModelSim DO files (wave, list)	One tb.vhd for the Datapath
		One tb.vhd for the Control unit
		One tb.vhd for the overall DUT (with Datatpath and
		Control unit signals included)
DOC	Project documentation	• readme.txt (list of the DUT *.vhd files with their
		brief functional description)
		• <i>pre3.pdf</i> (report file that includes brief
		explanation of the top module with its wave
		diagrams as shown in figure 4)

Table 2: Directory Structure

 


Figure 4: Clouds over the waveform example

6. Grading Policy

Weight	Task	Description
10%	Documentation	The "clear" way in which you presented the requirements and the analysis and conclusions on the work you've done
90%	Analysis and Test	The correct analysis of the system (under the requirements)

Table 3 : Grading

Under the above policies you'll be also evaluated using common sense:

- Your files will be compiled and checked, the system must work.
- Your design and architecture must be intelligent, minimal, effective and well organized.

For a late submission the penalty is 2^{days}